Homework 1 EENG530 Fall 2018

Lewis Setter

August 30, 2018

1.1

$$Z_{0} = 75\Omega, l_{line} = 0.65\lambda$$

$$V_{g} = 5\angle 90^{\circ}, Z_{g} = 10 + j20\Omega$$

$$Z_{L} = 50\Omega$$

$$V_{line} = V(-l_{line}) - V(0)$$

$$V(-l_{line}) = V_{0}^{+}(e^{j\beta l_{line}} + \Gamma_{l}e^{-j\beta l_{line}})$$

$$= V_{0}^{+}(e^{j1.3\pi} + \Gamma_{l}e^{-j1.3\pi})$$

$$V(0) = V_{0}^{+}(1 + \Gamma_{l})$$

$$\Rightarrow V_{line} = V_{0}^{+}(e^{j1.3\pi} - 1 + \Gamma_{l}(e^{-j1.3\pi} - 1))$$

$$V_{0}^{+} = V_{g} \frac{Z_{0}}{Z_{0} + Z_{g}} \frac{e^{j\beta l_{line}}}{1 - \Gamma_{g}\Gamma_{l}e^{j2\beta l_{line}}}$$

$$= V_{g} \frac{Z_{0}}{Z_{0} + Z_{g}} \frac{e^{-j1.3\pi}}{1 - \Gamma_{g}\Gamma_{l}e^{-j2.6\pi}}$$

$$\Gamma_{l} = \frac{Z_{L} - Z_{0}}{Z_{L} + Z_{0}} = -0.2$$

$$\Gamma_{g} = \frac{Z_{g} - Z_{0}}{Z_{g} + Z_{0}} = 0.78\angle 150^{\circ}$$

$$\Rightarrow V_{0}^{+} = 3.8\angle - 163^{\circ}$$

$$\Rightarrow V_{line} = 6.1\angle 55^{\circ}$$

$$P = \frac{1}{2}|V_{g}|^{2} \frac{R_{in}}{(R_{in} + R_{g})^{2} + (X_{in} + X_{g})^{2}}$$

$$Z_{in} = Z_{0} \frac{Z_{L} + jZ_{0} \tan \beta l_{line}}{Z_{0} + jZ_{L} \tan \beta l_{line}}$$

$$= Z_{0} \frac{Z_{L} + jZ_{0} \tan 1.3\pi}{Z_{0} + jZ_{L} \tan 1.3\pi}$$

$$= 79 + j31\Omega$$

$$\Rightarrow P = 0.094$$

$$\Gamma = 0.31 + j0.28$$


$$\Gamma_{l=0.4\lambda} = -0.24 + j0.34$$

$$SWR = 2.4$$

$$Z_{in} = (0.56 + j0.5)(50\Omega) = 28 + j25\Omega$$

The Complete Smith Chart

Black Magic Design

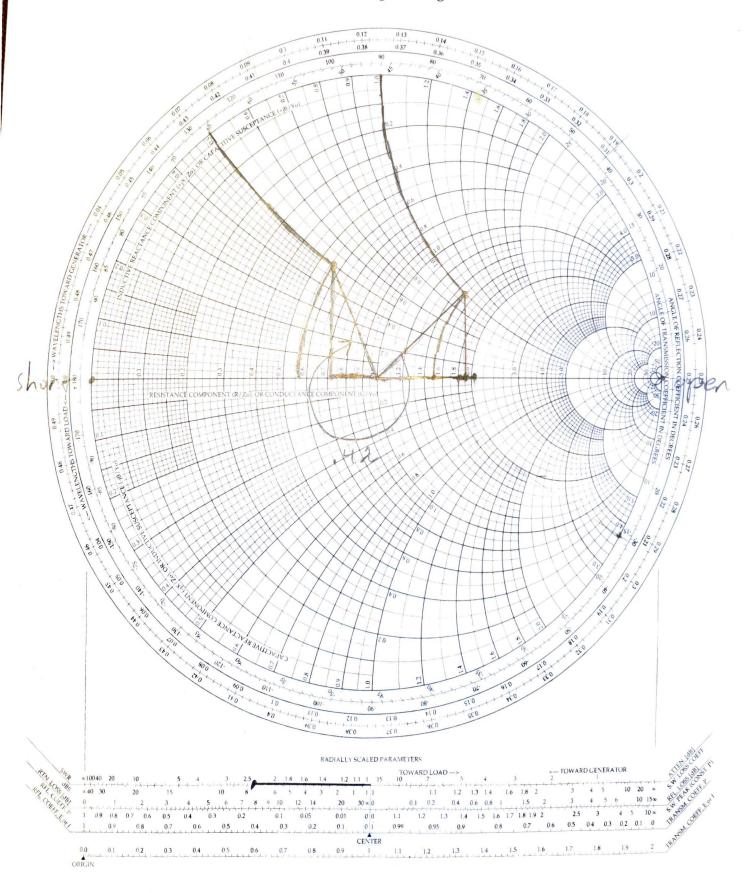

```
W ZinSITL: plot Z_in for a simi-infinite transmission line carrying a sinusoid
%
% user specified variables:
%
    - Z<sub>-0</sub>: charcteristic impedance of the line

    l: length of the line wavelengths of the transmitted wave
    Z.L: load impedance

%
%
% usage:
% When a user sets the specified inputs, the program produces plots
% of the magnitue and phase of the input impedance of a corresponding
% semi inifinite transmission line up to the desired length.
% user specified inputs
Z_{-0} = 50; 1 = 5; Z_{-L} = 10+j20;
% compute Z_in
lVals = 0:1/1000:1;
Z_{-in} = Z_{-0} * (Z_{-L} + 1j*Z_{-0}*tan(2*pi*lVals)) ./ (Z_{-0} + 1j*Z_{-L}*tan(2*pi*lVals));
% create plots
figure
subplot (2,1,1)
plot(lVals,abs(Z_in))
ylabel('|Z_{in}|')
subplot (2,1,2)
plot(lVals, angle(Z_in)*180/pi)
ylabel('\angle Z_{in}')
xlabel('\lambda from generator')
```

